

MANO BASIC COMPUTER

ENG \ Ali Khamis
ENG \ Fares Hazem
ENG \ Ahmed Mohamed
ENG \ Mahmoud Abdelsamad
ENG \ Saleh Gamal
ENG \ Abdallah Alsayed
ENG \ Ahmed Shehata

MODERATOR :

ENG \ Kame1 Mohamed

INTRODUCTION


- *The Mano basic computer is a classic example of a simple computer architecture. It is a 16-bit computer.*
- *The Mano basic computer consists of several main components, including a central processing unit , memory, and a clock.*
- *We used verilog language to program this project*

VERILOG

- *Once we have created the necessary modules, we can simulate the behavior of the Mano basic computer using a Verilog simulator. This allows us to test the functionality of the computer and verify that it operates as expected. We can also use Verilog to synthesize the design into actual hardware, which can be programmed onto a field programmable gate array (FPGA) or other hardware platform*

INSTRUCTION CODE & DESIGN

 
- *01 Sequence counter*
- *02 Memory*
- *03 Register*
- *04 Control Register*
- *05 ALU*



```

1  module SC_Control(CLR, T, D,I,B,S);
2
3      output CLR,S;
4      input [7:0] T, D;
5      input I;
6      input [15:0] B;
7
8      wire a1, a2, a3, a4, a5, o1, o2;
9      wire r,In;
10
11     assign I=~I ;
12     assign r= D[7] & T[3] &In;
13     assign o1 = D[4] | D[3];
14     assign a1 = o1 & T[4];
15     assign a2 = D[7] & T[3];
16     assign a3 = D[6] & T[6] ;
17     assign o2 = D[2] | D[1] | D[0] | D[5];
18     assign a4 = o2 & T[5];
19     assign CLR = a1 | a2 | a3 | a4 ;
20     assign S= B[0] & r;
21 endmodule

```

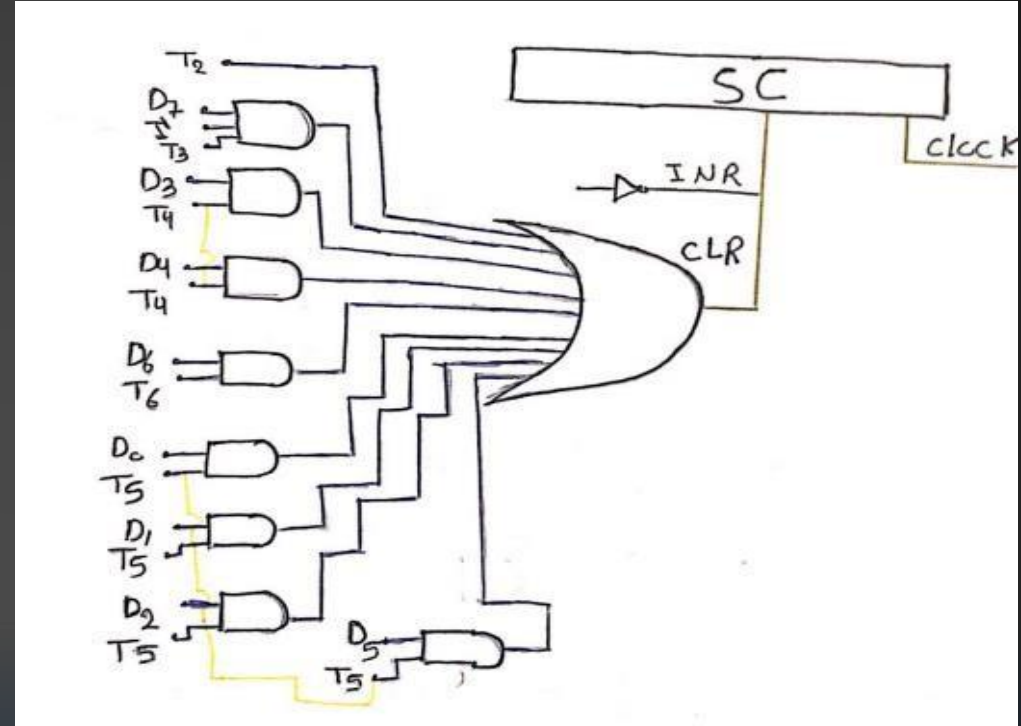

SEQUENCE COUNTER


```

module RAM (CLK, read, AR, write, INDATA, OUTDATA );
    input CLK, read, write;
    input [15:0] INDATA;
    input [11:0] AR;
    output reg [15:0] OUTDATA;

    reg [15:0] RAM_4K [4096:0];

    initial
    begin
        RAM_4K[0] = 16'h7020;      //clear AC
        RAM_4K[1] = 16'h7800;      //clear AC
        RAM_4K[2] = 16'h7200;      //CMA
        RAM_4K[3] = 16'h2004;      //LDA
        RAM_4K[4] = 16'h2002;      //ADD
        RAM_4K[5] = 16'h7001;      //HLT
    end

    always@* begin
        if (write)
            RAM_4K[AR] <= INDATA;
        else if (read)
            OUTDATA = RAM_4K[AR];
        end
    end
endmodule

```


MEMORY

```

1  module Memory_Control(Str, Load, T, D, I);
2
3      input  I;
4      input [7:0] T, D;
5      output Str, Load;
6
7      wire Dn7;
8      wire A2, A3, A4, A5, A6, A7, A8, A9;
9
10     assign Dn7 = ~D[7];
11     assign A3 = D[3] & T[4];
12     assign A4 = D[5] & T[4];
13     assign A5 = D[6] & T[6];
14     assign A6 = Dn7 & I & T[3];
15     assign A7 = D[6] & T[4];
16     assign A9 = D[2] | D[1] | D[0];
17     assign A8 = A9 & T[4];
18     assign Str = A3 | A4 | A5;
19     assign Load = T[1] | A6 | A7 | A8;
20
21 endmodule

```

MEMORY CONTROL

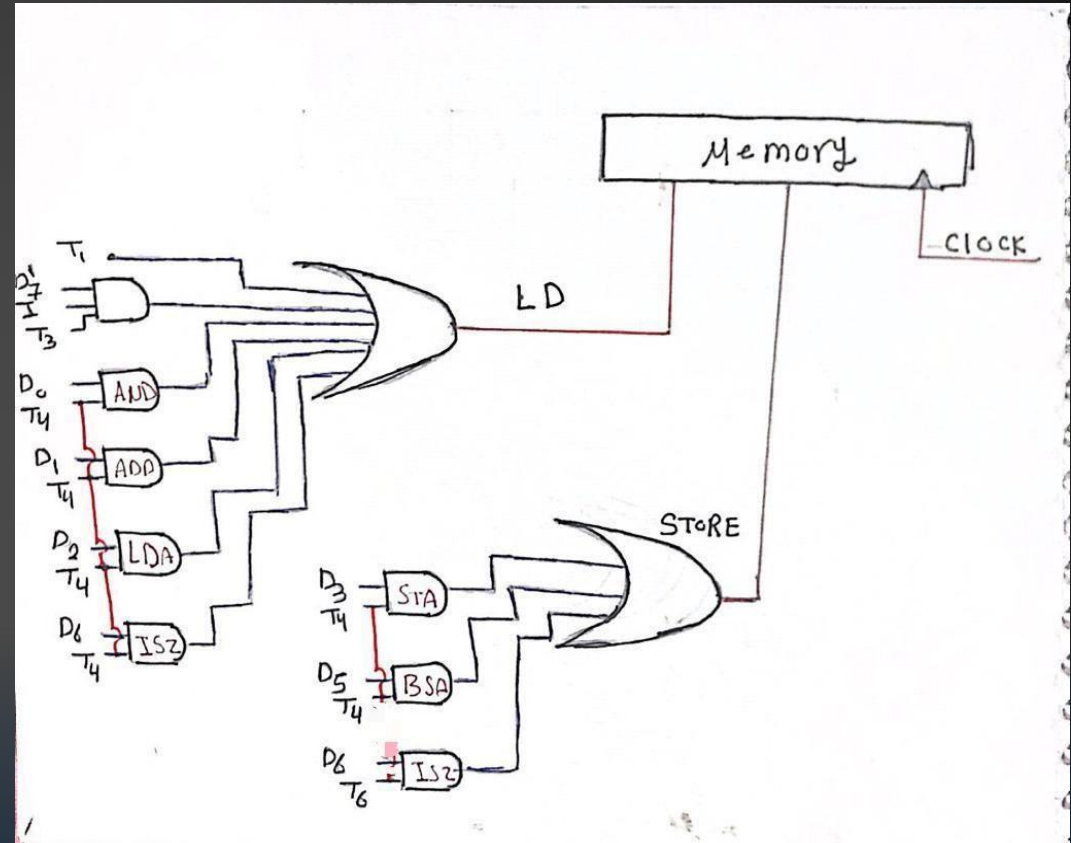

DESIGN

REGISTERS

✓ ***AR REGISTER***

✓ ***PC REGISTER***

✓ ***DC REGISTER***

✓ ***AC REGISTER***

AR Register

```
module REG_11(Q, INR, Data, LD, CLK, CLR);  
  
    output reg [11:0] Q;  
    input [11:0] Data;  
    input INR, LD, CLK, CLR;  
  
    initial Q = 0;  
  
    always @(posedge CLK)  
    begin  
        if(CLR)  
            Q <= 16'b0;  
        else if(LD)  
            Q <= Data;  
        else if(INR)  
            Q <= Q + 1;  
    end  
endmodule
```

Pc Register

```
module REG_11(Q, INR, Data, LD, CLK, CLR);  
  
    output reg [11:0] Q;  
    input [11:0] Data;  
    input INR, LD, CLK, CLR;  
  
    initial Q = 0;  
  
    always @(posedge CLK)  
    begin  
        if(CLR)  
            Q <= 16'b0;  
        else if(LD)  
            Q <= Data;  
        else if(INR)  
            Q <= Q + 1;  
    end  
endmodule
```

DR Register

```
module REG_11(Q, INR, Data, LD, CLK, CLR);  
  
    output reg [11:0] Q;  
    input [11:0] Data;  
    input INR, LD, CLK, CLR;  
  
    initial Q = 0;  
  
    always @(posedge CLK)  
    begin  
        if(CLR)  
            Q <= 16'b0;  
        else if(LD)  
            Q <= Data;  
        else if(INR)  
            Q <= Q + 1;  
        end  
    end  
endmodule
```

Ac Register


```
module REG_16(Q, INR, Data, LD, CLK, CLR);  
  
    initial Q = 0;  
  
    output reg [15:0] Q;  
    input [15:0] Data;  
    input INR, LD, CLK, CLR;  
  
    always @(posedge CLK)  
    begin  
        if(CLR)  
            Q <= 16'b0;  
        else if(LD)  
            Q <= Data;  
        else if(INR)  
            Q <= Q + 1;  
    end  
endmodule
```

CONTROL REGISTERS

AR CONTROL

```
1 module AR_Control(LD, CLR, INR, T, D, I);
2
3     input I;
4     input [7:0] T, D;
5     output LD, CLR, INR;
6
7     wire D7n, Rn;
8     wire a1, a2, a3;
9
10    assign D7n = ~D[7];
11
12    assign a1 = D7n & I & T[3];
13    assign a2 = T[2] & Rn;
14    assign a3 = Rn & T[0];
15    assign CLR = T[0];
16    assign INR = D[5] & T[4];
17    assign LD = a1 | a2 | a3;
18
19 endmodule
```

DESIGN

 


PC CONTROL

```

2 module PC_control(CLR, INR, Load, I, E, T, D, B, DR, AC);
3     output CLR, INR, Load;
4     input I, E;
5     input [7:0] T, D;
6     input [15:0] B;
7     input [15:0] DR, AC;
8
9     wire In, AC15n, En, a1, a3, r, p, a6, a7, a8, a9, a10, o1, a11, o2;
10    wire a15, a16;
11
12    assign In= ~I;
13    assign AC15n=~AC[15];
14    assign En=~E;
15    assign a1= T[1];
16    assign CLR=T[1];
17    assign a3= T[2];
18    assign p= I & T[3] & D[7];
19    assign r= In & D[7] & T[3];
20    //
21    //
22    //
23    assign a8 = B[3] & AC[15]; //SNA
24    assign a9 = AC15n & B[4]; //SPA
25    assign a10 = En & B[1]; //SZE
26    assign o1 = a8 | a9 | a10;
27    assign a11 = r & o1; // all SNA , SPA , SZE
28
29
30    assign Load = a15 | a16; // if one of these conditions is true then pc = load
31    assign INR = a1 | a3 | a11 | p; // if one of these conditions is true then pc <= pc
32
33 endmodule

```


DESIGN

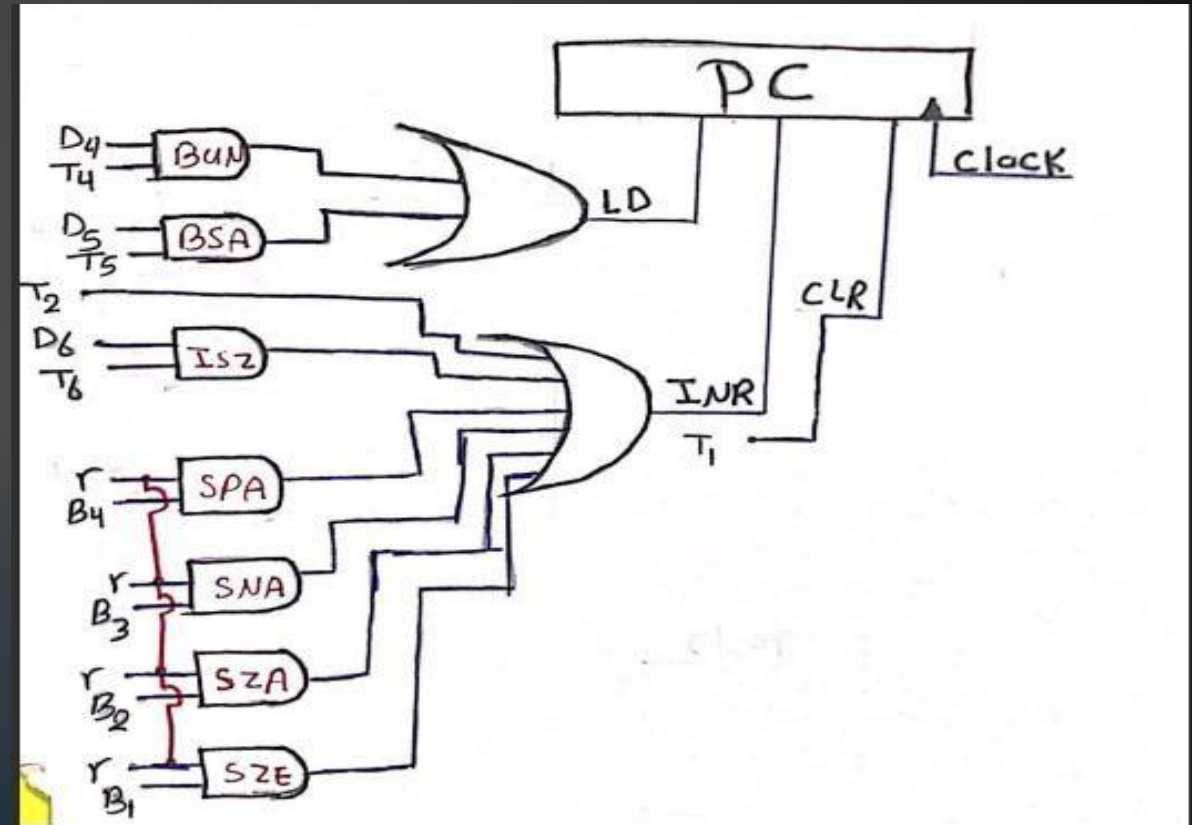

DR CONTROL

```
1 module DR_Control(Load, INR, T, D);  
2  
3     input [7:0] T,D;  
4     output Load, INR;  
5  
6     wire ToLoad;  
7  
8     assign INR = D[6] & T[5];  
9     assign ToLoad = (D[0] | D[1] | D[2] | D[6]);  
10    assign Load = T[4] & ToLoad;  
11  
12 endmodule
```

DESIGN

 


AC CONTROL

```

1 module AC_Control(AND, COM, SHR, SHL, INPT, DR, ADD, LD, INR, CLR, T, D, B, I);
2
3     output AND, SHR, SHL, COM, INPT, DR, ADD, LD, INR, CLR;
4     input[7:0] T, D;
5     input[15:0] B;
6     input I;
7
8     wire In;
9     wire r, p;
10    assign In = ~I;
11
12    assign p = D[7] & I & T[3];
13    assign r = D[7] & In & T[3];
14
15    assign AND = D[0] & T[5];
16    assign ADD = T[5] & D[1];
17    assign DR = T[5] & D[2];
18    assign COM = B[9] & r;
19    assign SHL = B[6] & r;
20    assign SHR = B[7] & r;
21    assign INR = B[5] & r;
22    assign INPT = B[11] & p;
23
24    assign LD = (AND | ADD | DR | SHL | SHR | COM | INPT);
25    assign CLR = r & B[11];
26 endmodule
    
```

DESIGN

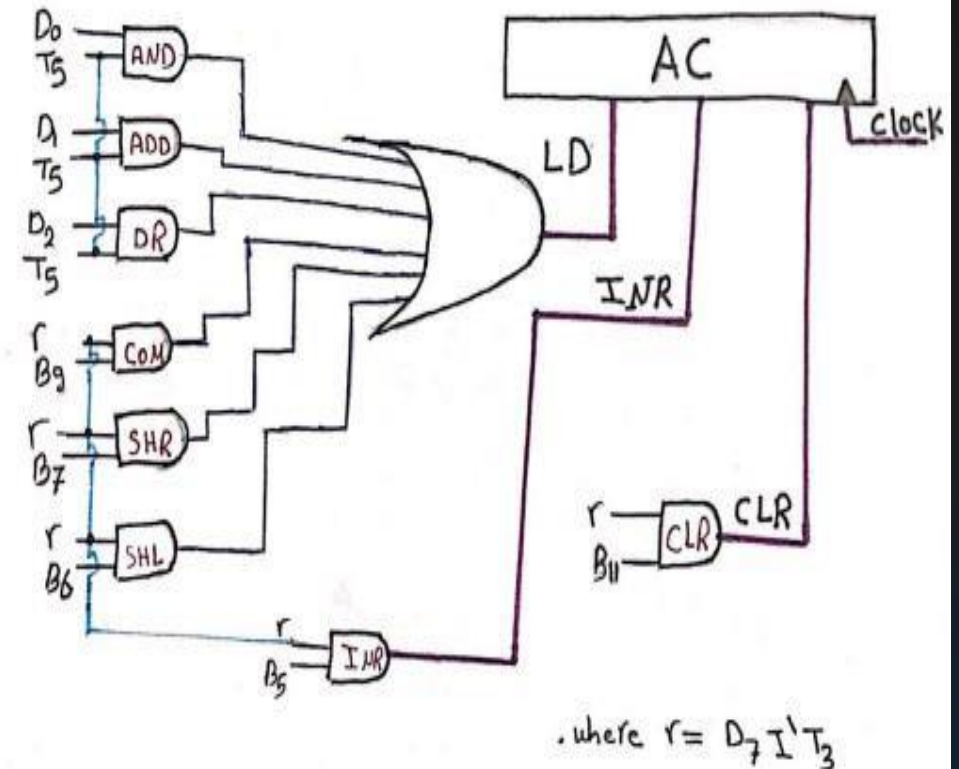

ALU

```
module ALU(AND,ADD, LDA, CMA,E,AC, DR,cout , ACDATA);
    input AND,ADD, LDA, CMA,E;      //instructions signals
    input [15:0] AC, DR;
    output cout ;
    output [15:0] ACDATA;

    wire [15:0] and16,add16,lda16,cma16;      // turning the instructions signals into 16-bit signal to be anded
    wire [15:0] AND1,AND2,AND3,AND4 ,SUM;      //AND gate of each instruction
    wire CARRY;

    //AND OPERATION
    assign and16 = (AND ? 16'hffff :16'b0);
    assign AND1 = AC & and16 & DR;

    //ADD OPERATION , {CARRY,SUM} is the result of a full-adder
    assign {CARRY,SUM} = AC + DR ;
    assign cout = CARRY;

    assign add16 = (ADD ? 16'b1111111111111111 :16'b0);
    assign AND2 = SUM & add16 ;

    //LDA OPERATION (load AC with DR content )
    assign lda16 = (LDA ? 16'hffff :16'b0);
    assign AND3 = lda16 & DR ;

    //CMA OPERATION (Complement AC content)
    assign cma16 = (CMA ? 16'hffff : 16'b0);
    assign AND4 = (~AC) & cma16;
    wire o1 ,o2;

    assign ACDATA = AND1 | AND2 | AND3 | AND4;      // All AND gates signals to be into an OR gate that results in AC
endmodule
```


Name	Value	60 ns	70 ns	80 ns	90 ns	100 ns	110 ns	120 ns	130 ns	140 ns	150 ns	160 ns	170 ns	180 ns						
DR[15:0]	0000	0000													2002					
AC[15:0]	0001	000	ffff													2002				
IR[15:0]	7800	7800	7200													2004				
MEM[15:0]	7800	7800	7200													2004	2002			
PC[11:0]	002	002	003													004				
AR[11:0]	800	001	800	002	200													003	004	
T[7:0]	08	04	08	01	02	04	08	01	02	04	08	10	20	01						
D[7:0]	80	80													04					
outsq[2:0]	3	1	2	3	0	1	2	3	0	1	2	3	4	5	0					
Data[15:0]	7800	7800	0002	7200													0003	2004	2002	0004
X[7:0]	00	20	00	04	80	20	00	04	80	20	00	80	08	04						
I	0																			
E	0																			
CLK	1	0																		